

Fig. 4. Circuit of Fig. 3 in block schematic form.

scribed. The pentode section used for the first stage provides considerably higher gain than the triode used as an example in describing the operation of the circuit. R_{26} adjusts operating bias for the first stage, and should be set at approximately 2 volts. R_7 adjusts for a.c. balance of the phase splitter, and once R_{26} and R_7 have been adjusted, they usually retain the adjustment indefinitely. C_4 should have a value of 1500 μf , and C_8 should be 82 μf ; there is no C_7 or C_9 . R_{20} has a value of 750 ohms for the transformer specified when working

at 16 ohms. The transformer may not be critical to the circuit, but as with any tetrode or pentode power amplifier using feedback, the components in the feedback circuit may require adjustment with a square-wave generator and an oscilloscope. The screens of the two 6AN8's should be operated at 60 to 62 volts, while the plates should measure around 95 volts. At the power supply, the output-stage tap is 470 volts; the plates of the triode sections of the 6AN8's should be 410 volts, and the voltage at the junction of R_3 and R_5 should be 300 to 310 volts. Bias on the output stage measures at 37 volts on the grids, and is adjusted by R_{22} ; R_{12} balances the plate current in the two output tubes. It may be necessary to select two 6AN8's to get a good balance between them, but once balanced they should remain so.

There is no reason why this amplifier could not be constructed with output transformers other than the one specified, but the characteristics of transformers vary appreciably, and some of the circuit constants would have to be readjusted.

In layout, it is important that leads should be as short as possible. The coupling capacitors leading from the cathode followers should go direct to the output stages without crowding to ensure a good capacitive balance. It is desirable that the a.c. balance control, R_7 , be located between the phase splitter tubes, and R_{26} should be close enough so that R_{24} runs directly between the arms of the two pots.

Performance

Measured IM distortion on the amplifier was below 0.2 per cent up to 30 watts, reaching 0.6 per cent at 45 watts, and 2 per cent at 51 watts. Frequency response is within ± 0.5 db from 10 to 10,000 cps (for the phase splitter alone it remained balanced and "flat" to over 1 mc). An input signal of 2 volts is necessary to overcome the very heavy feedback and drive the amplifier to a 50-watt output.

The amplifier described—as well as the phase splitter itself—is not commercially available, but its performance makes it well worthy of investigation by the advanced experimenter. Æ

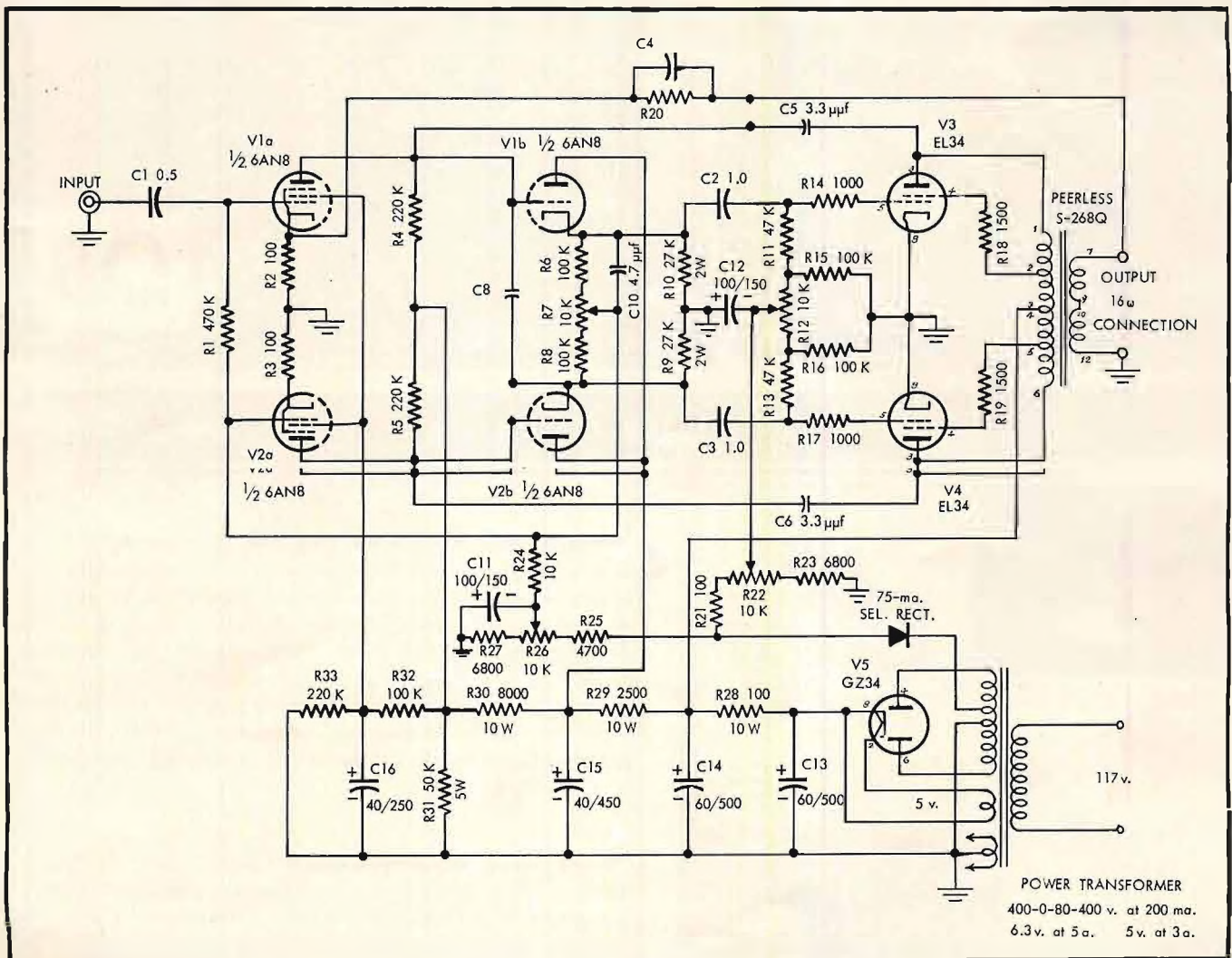


Fig. 5. The complete amplifier using a pair of EL34's in the output stage reaches a new low in distortion and unbalance.