

LM2408

LM2408 Monolithic Triple 4.5 ns CRT Driver



Literature Number: SNOS811A

LM2408 Monolithic Triple 4.5 ns CRT Driver

Features

- Rise/fall times typically 4.5 ns with 8 pF load
- Output swing capability: 50 V_{PP} for V_{CC} = 80
40 V_{PP} for V_{CC} = 70
30 V_{PP} for V_{CC} = 60

- Pinout designed for easy PCB layout
- 1V to 7V input range
- Stable with 0 pF–20 pF capacitive loads
- Convenient TO-220 staggered lead package style

- CRT driver for 1280×1024 (Non-interfaced) and XGA display resolution color monitors
- Pixel clock frequency up to 160 MHz

The diagram shows a complex CMOS logic circuit with the following components and connections:

- Input Stage:** An input terminal connects to the gate of transistor Q1. The source of Q1 is grounded. The drain of Q1 is connected to the gate of transistor Q2. The source of Q2 is grounded. The drain of Q2 is connected to the gate of transistor Q3.
- Second Stage:** Transistor Q3 has its source grounded and its drain connected to the gate of transistor Q4. The source of Q4 is grounded. The drain of Q4 is connected to the gate of transistor Q5.
- Third Stage:** Transistor Q5 has its source grounded and its drain connected to the gate of transistor Q6. The source of Q6 is grounded. The drain of Q6 is connected to the gate of transistor Q8.
- Current Source and Load:** Transistor Q9 is a PMOS transistor with its gate connected to V_{BB} and its source connected to the drain of Q2. Its drain is connected to the gate of Q8. Transistor Q8 is a PMOS transistor with its gate connected to V_{CC} and its source connected to the drain of Q6. Its drain is connected to the gate of Q5.
- Output Stage:** Transistor Q5 has its source connected to the drain of Q6. The drain of Q5 is connected to the output terminal. Transistor Q6 has its source grounded and its drain connected to the output terminal.
- Power and Biasing:** The circuit is powered by V_{CC} and V_{BB}. V_{CC} is connected to the gates of Q8 and Q5. V_{BB} is connected to the gates of Q9 and Q6. A 15k resistor is connected between V_{BB} and the gate of Q9. A 1k resistor is connected between the gate of Q2 and the gate of Q9.

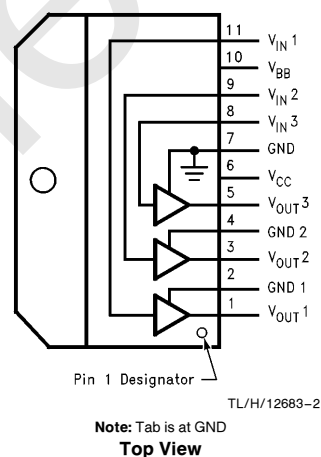


FIGURE 1. Simplified Schematic Diagram (One Channel)

Absolute Maximum Ratings

(Notes 1 and 3)

Supply Voltage (V_{CC})	+95V
Bias Voltage (V_{BB})	+16V
Input Voltage (V_{IN})	-0.5V to $V_{BIAS} + 0.5V$
Storage Temperature Range (T_{STG})	-65°C to +150°C
Lead Temperature (Soldering, <10 sec.)	300°C
ESD Tolerance	2 kV

Operating Ranges (Note 2)

V_{CC}	+60V to +85V
V_{BB}	+8V to +15V
V_{IN}	+1V to +7V
Case Temperature (T_{CASE})	-20°C to +100°C

Do not operate the part without a heat sink.

Electrical Characteristics

Unless otherwise noted: $V_{CC} = +80V$, $V_{BB} = +12V$, $V_{IN} = +3.2V$ (at LM2408 input pins), $C_L = 8\text{ pF}$, Output = 40 V_{PP} at 1 MHz, $T_A = 25^\circ\text{C}$.

Symbol	Parameter	Conditions	LM2408			Units
			Min	Typical	Max	
I_{CC}	Supply Current	Per Channel, No Output Load		22	30	mA
I_{BB}	Bias Current			21		mA
V_{OUT}	DC Output Voltage	No Input Signal	47	50	53	V _{DC}
A_V	DC Voltage Gain	No Input Signal	-13	-15	-17	
ΔA_V	Gain Matching	(Note 4)		1.0		dB
LE	Linearity Error	(Notes 4, 5)		8		%
t_R	Rise Time	10% to 90%, $f = 1\text{ MHz}$		4.5		ns
t_F	Fall Time	90% to 10%, $f = 1\text{ MHz}$		4.5		ns

Note 1: Absolute Maximum Ratings indicate limits beyond which damage to the device may occur.

Note 2: Operating ratings indicate conditions for which the device is functional, but do not guarantee specific performance limits. For guaranteed specifications and test conditions, see the Electrical Characteristics. The guaranteed specifications apply only for the test conditions listed. Some performance characteristics may change when the device is not operated under the listed test conditions.


Note 3: All voltages are measured with respect to GND, unless otherwise specified.

Note 4: Calculated value from Voltage Gain test on each channel.

Note 5: Linearity Error is defined as the variation in DC gain from $V_{IN} = +1.90V$ to $V_{IN} = +4.50V$.

Note 6: Input from signal generator: $t_R, t_F < 1\text{ ns}$.

AC Test Circuit

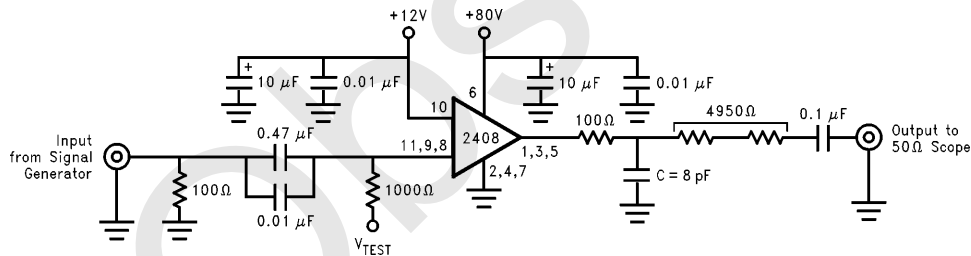

TL/H/12683-3

Note: 8 pF is total load plus parasitic capacitance.

Note: Adjust V_{TEST} for +3.2V DC at LM2408 input pins.

FIGURE 2. Test Circuit (One Channel)

Figure 2 shows a typical test circuit for evaluation of the LM2408. This circuit is designed to allow testing of the LM2408 in a 50Ω environment, such as a pulse generator,

oscilloscope or network analyzer. The 4950Ω resistor at the output forms a 100:1 voltage divider when connected to a 50Ω load.

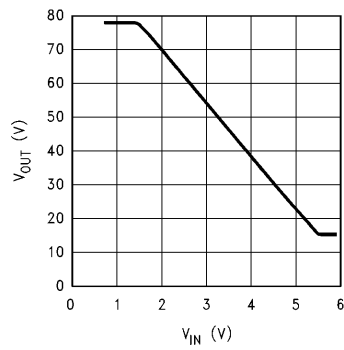


FIGURE 3. V_{OUT} vs V_{IN}

TL/H/12683-4

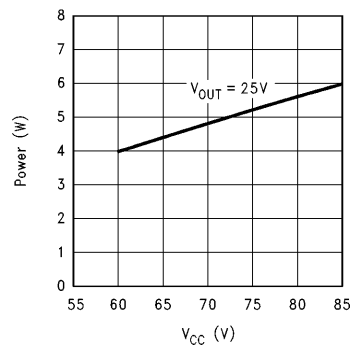


FIGURE 4. Power Dissipation vs V_{CC}

TL/H/12683-5

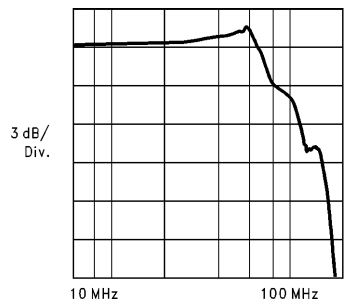


FIGURE 5. Large Signal Frequency Response

TL/H/12683-6

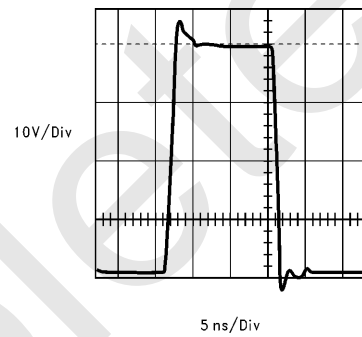


FIGURE 6. Pulse Response

TL/H/12683-7

Theory of Operation

The LM2408 is a high voltage monolithic triple CRT driver suitable for SVGA and XGA display applications. The LM2408 features +80V operation and low power dissipation. The part is housed in the industry standard 11-Lead TO-220 molded plastic power package.

The simplified circuit diagram of the LM2408 is shown in Figure 1. A PNP emitter follower, Q1, provides input buffering. Q2 and Q3 form a high gain amplifier. Feedback around this amplifier through the 15 k Ω resistor, working with the 1 k Ω input resistor, sets the gain to -15 . Emitter followers Q5 and Q6 isolate the high output impedance of the amplifier from the capacitance of the CRT cathode, and make the circuit relative insensitive to load capacitance.

Figure 2 shows a typical test circuit for evaluation of the LM2408. This circuit is designed to allow testing of the LM2408 in a 50 Ω environment, such as a pulse generator and a scope, or a network analyzer. In this test circuit, two low inductance resistors in series totaling 4.95 k Ω form a 100:1 wideband low capacitance probe when connected to a 50 Ω cable and load. The input signal from the generator is AC coupled to the base of Q1.

Application Hints

INTRODUCTION

National Semiconductor is committed to providing application information that assists our customers in obtaining the best performance possible from our products. The following information is provided in order to support this commitment. The reader should be aware that the optimization of performance was done using specific printed circuit boards designed at National. Variations in performance can be realized due to physical changes in the printed circuit board and the application. Therefore, the designer should be aware that component value and board layout changes may be required to optimize performance in a given application. The values shown in this document can be used as a starting point for testing and evaluation purposes. When working with high bandwidth circuits, good layout practices are also critical to achieving maximum performance.

POWER SUPPLY BYPASS

Since the LM2408 is a wide bandwidth amplifier, proper power supply bypassing is critical for optimum performance. Improper power supply bypassing can result in large overshoot, ringing and oscillation. A 0.01 μ F capacitor should be connected from the supply pin, V_{CC} , to ground, as close to the supply pin as is practical (preferably less than $\frac{1}{4}$ " from the supply pin). Additionally, a 10 μ F to 100 μ F electrolytic capacitor should be connected from the supply pin to ground. The electrolytic capacitor should also be placed reasonably close to the LM2408's supply pin. A 0.1 μ F capacitor should be connected from the bias pin, V_{BB} , to ground, as close as is practical to the part.

ARC PROTECTION

During normal CRT operation, internal arcing may occasionally occur. Spark gaps of 200V to 300V at the cathodes will limit the maximum voltage, but to a value that is much high-

er than allowable on the LM2408. This fast, high voltage, high energy pulse can damage the LM2408 output stage. The addition of clamp diodes D1 and D2 (as shown in Figure 7) will help clamp the voltage at the output of the LM2408 to a safe level. The clamp diodes should have a fast transient response, high peak current rating, low series impedance and low shunt capacitance. FDH400 or equivalent diodes are recommended. Resistor R2 in Figure 7 limits the arcover current while R1 limits the current into the LM2408 and reduces the power dissipation of the output transistors when the output is stressed beyond the supply voltage. Peaking inductor L_p also helps protect the LM2408 from CRT arcover, and is part of the arc protection circuit. Having large value resistors for R1 and R2 would be desirable, but this has the effect of increasing rise and fall times. For proper arc protection, it is important to not omit any of the arc protection components shown in Figure 7.

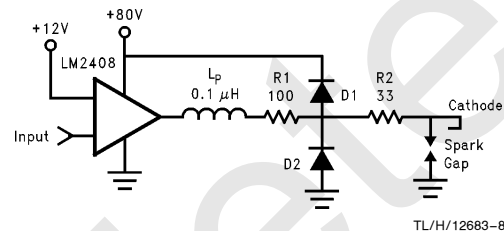


FIGURE 7. One Section of the LM2408 with Arc Protection and Peaking Inductor L_p

There are also ESD protection diodes built into the part. To avoid damaging these diodes, do not apply an input voltage from a low impedance source when the V_{BB} and V_{CC} pins are held at ground potential.


IMPROVING RISE AND FALL TIMES

Because of an emitter follower output stage, the rise and fall times of the LM2408 are relatively insensitive to capacitive loading. However, the series resistors R1 and R2 (see Figure 7) will increase the rise and fall times when driving the CRT's cathode which appears as a capacitive load. The capacitance at the cathode typically ranges from 8 pF to 12 pF.

To improve the rise and fall times at the cathode, a small inductor is often used in series with the output of the amplifier. The inductor L_p in Figure 7 peaks the amplifier's frequency response at the cathode, thus improving rise and fall times. It also acts with the output load capacitance to form a low pass filter, which reduces the amplitudes of high frequency harmonics of the video signal, to lower radiated electromagnetic interference. The inductor value is empirically determined and is dependent on the load. An inductor value of 0.1 μ H is a good starting value. Note that excessive peaking of the amplifier's frequency response will increase the overshoot. Choosing the correct values for R1, R2 and L_p will provide arc protection and the fastest rise and fall times without excessive peaking.

EFFECT OF LOAD CAPACITANCE

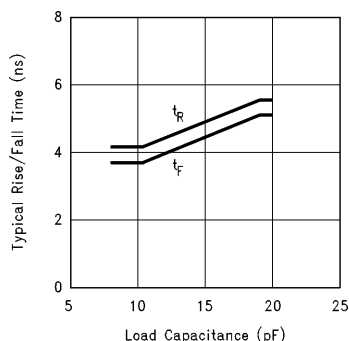The output rise and fall times will be slower than specified if the load capacitance at the output is more than 8 pF, as shown in *Figure 8*.



TL/H/12683-9

FIGURE 8. Effect of Load Capacitance on Rise/Fall Time

The monitor designer should ensure that stray capacitance applied to the LM2408 is as low as possible.

THERMAL CONSIDERATIONS

Power supply current increases as the input signal increases and consequently power dissipation also increases.

The LM2408 cannot be used without heat sinking. Typical "average" power dissipation with the device output voltage at one half the supply voltage is 1.9W per channel for a total dissipation of 5.7W package dissipation. The power dissipation does not vary much as output voltage varies. The LM2408 case temperature must be maintained below 100°C. If the maximum expected ambient temperature is 50°C, then a maximum heat sink thermal resistance can be calculated:

$$R_{th} = \frac{100^{\circ}\text{C} - 50^{\circ}\text{C}}{5.7\text{W}} = 8.8^{\circ}\text{C/W}.$$

This example assumes a typical CRT capacitive load and is without a resistive load. Note that this thermal resistance must be achieved when the heat sink is operating in the monitor.

PC BOARD LAYOUT CONSIDERATIONS

For optimum performance, an adequate ground plane, isolation between channels, good supply bypassing and minimizing unwanted feedback are necessary. Also, the length of the signal traces from the preamplifier to the LM2408 and from the LM2408 to the CRT cathode should be as short as possible. The following references are recommended:

Ott, Henry W., "Noise Reduction Techniques in Electronic Systems", John Wiley and Sons, New York, 1976.

"Guide to CRT Video Design", National Semiconductor Application Note 861.

"Video Amplifier Design for Computer Monitors", National Semiconductor Application Note 1013.

Because of its high small signal bandwidth, the part may oscillate when it is used in a typical application with a preamp in a monitor, if feedback occurs around the video amplifier through the chassis wiring. To prevent this, leads to the input circuit should be shielded, and input circuit wiring should be spaced as far as possible from output circuit wiring. Power should be removed as quickly as possible from an amplifier that is oscillating, since power dissipation in the part is very high in this mode and the part may be damaged if oscillations continue and the power supply can supply more than 250 mA.

Capacitive loading on the output will cause some overshoot and peaking. This can be controlled by placing a resistor in series with the output of the part. Because of differences in stray capacitance in different pc board layouts, the best value of resistance to use must be determined separately for each application. Typical values between 50Ω and 200Ω provide good performance, with the larger values resulting in less peaking and slower rise and fall times.

Driving the output voltage of the part outside of its linear range will cause distorted signal waveforms and recovery times that are very much longer than the specified rise and fall times. When the amplifier output voltage is being driven from positive saturation into the linear range, an overshoot of several volts for up to 50 ns may occur. In a typical monitor design, this may occur if blanking pulses are applied to the video signal. The output voltage range should be limited so this does not happen, and will be approximately no lower than 25V and no higher than $V_{CC} - 5V$.


TYPICAL APPLICATION

A typical application of the LM2408 is shown in *Figure 9*. Used in conjunction with an LM1205, a complete video channel from monitor input to CRT cathode can be achieved. Performance is satisfactory for all applications up to 1280 × 1024 non-interlaced, and pixel clock frequencies up to 160 MHz.

Obsolete

LM2408 Monolithic Triple 4.5 ns CRT Driver

Physical Dimensions inches (millimeters) unless otherwise noted

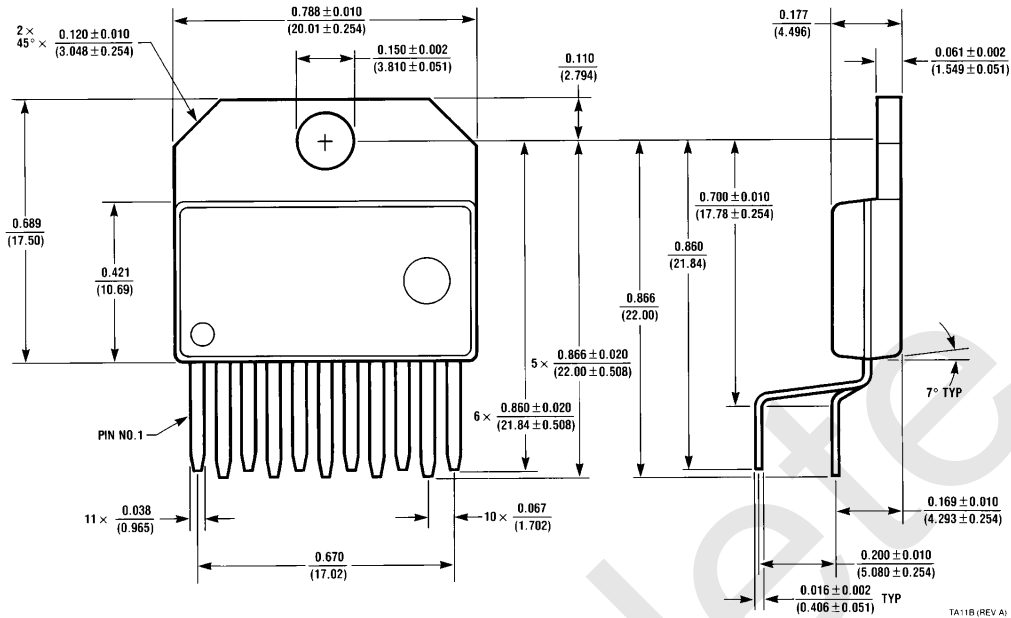

LM2408
11-Lead Molded TO-220
NS Package Number TA11B

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



National Semiconductor Corporation
Americas
 Tel: 1(800) 272-9959
 Fax: 1(800) 737-7018
 Email: support@nsc.com

<http://www.national.com>

National Semiconductor Europe
 Fax: +49 (0) 180-530 85 86
 Email: europe.support@nsc.com
 Deutsch Tel: +49 (0) 180-530 85 85
 English Tel: +49 (0) 180-532 78 32
 Français Tel: +49 (0) 180-532 93 58
 Italiano Tel: +49 (0) 180-534 16 80

National Semiconductor Southeast Asia
 Fax: (852) 2376 3901
 Email: sea.support@nsc.com

National Semiconductor Japan Ltd.
 Tel: 81-3-5620-7561
 Fax: 81-3-5620-6179

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated