

STK401-040

AF Power Amplifier (Split Power Supply) (25W+25W min, THD = 0.4%)

Overview

The STK401-040 is a thick-film audio power amplifier IC belonging to a series in which all devices are pin compatible. This allows a single PCB design to be used to construct amplifiers of various output capacity simply by changing hybrid ICs. Also, this series is part of a new, larger series that comprises mutually similar devices with the same pin compatibility. This makes possible the development of a 2-channel amplifier from a 3-channel amplifier using the same PCB. In addition, this new series features $6/3\Omega$ drive in order to support the low impedance of modern speakers.

Features

• Pin compatible STK400-000 series (3-channel/single package)


STK401-000 series (2-channel/single package)

- Output load impedance $R_L = 6/3\Omega$ supported
- New pin configuration
 Pin configuration has been grouped into individual blocks of inputs, outputs and supply lines, minimizing the adverse effects of pattern layout on operating characteristics.
- Few external components
 In comparison with existing series, external bootstrap resistors and capacitors can be eliminated.

Package Dimensions

unit: mm

4134

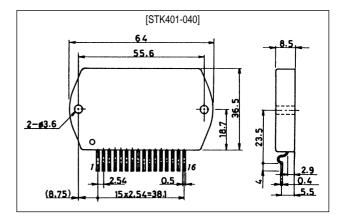

Specifications

Maximum Ratings at Ta = 25°C

Parameter	Symbol	Conditions	Ratings	Unit
Maximum supply voltage	V _{CC} max		±36	V
Thermal resistance	Өј-с	Per power transistor	2.1	°C/W
Junction temperature	Tj		150	°C
Operating substrate temperature	Tc		125	°C
Storage temperature	Tstg		-30 to +125	°C
Available time for load short-circuit	t _s	$V_{CC} = \pm 25V, R_L = 6\Omega,$ f = 50Hz, $P_O = 25W$	1	S

Operating Characteristics at Ta = 25°C, $R_L = 6\Omega$ (noninductive load), $Rg = 600\Omega$, VG = 40dB

Parameter	Symbol	Conditions	min	typ	max	Unit
Quiescent current	Icco	V _{CC} = ±30V	20	60	100	mA
Output power	P _O (1)	V _{CC} = ±25V, f = 20Hz to 20kHz, THD = 0.4%	25	30	-	W
Output power	P _O (2)	$V_{CC} = \pm 21V, f = 1kHz,$ THD = 1.0%, R _L = 3 Ω	25	30	_	W
Total harmonic distortion	THD(1)	$V_{CC} = \pm 25V$, f = 20Hz to 20kHz, $P_O = 1.0W$	-	_	0.4	%
Total Harmonic distortion	THD(2)	$V_{CC} = \pm 25V, f = 1kHz,$ $P_0 = 5.0W$	_	0.02	-	%
Frequency response	f _L , f _H	$V_{CC} = \pm 25V, P_O = 1.0W, ^{+0}_{-3} dB$	-	20 to 50k	-	Hz
Input impedance	r _i	$V_{CC} = \pm 25V, f = 1kHz,$ $P_0 = 1.0W$	_	55	_	kΩ
Output noise voltage	V _{NO}	$V_{CC} = \pm 30V$, Rg = $10k\Omega$	-	_	1.2	mVrms
Neutral voltage	V _N	V _{CC} = ±30V	-70	0	+70	mV


Notes.

All tests are measured using a constant-voltage supply unless otherwise specified.


Available time for load short-circuit and output noise voltage are measured using the transformer supply specified below.

The output noise voltage is the peak value of an average-reading meter with an rms value scale (VTVM). A regulated AC supply (50Hz) should be used to eliminate the effects of AC primary line flicker noise.

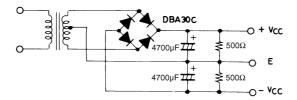
Specified Transformer Supply (RP-25 or Equivalent)



Equivalent Circuit

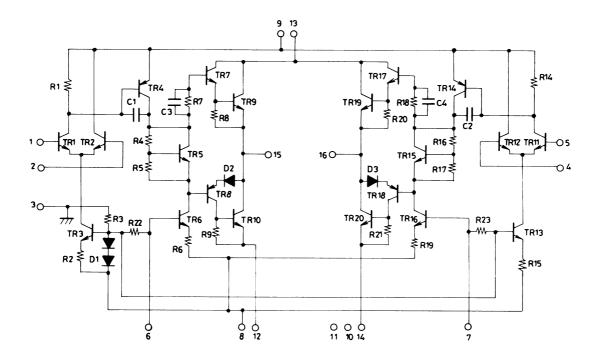


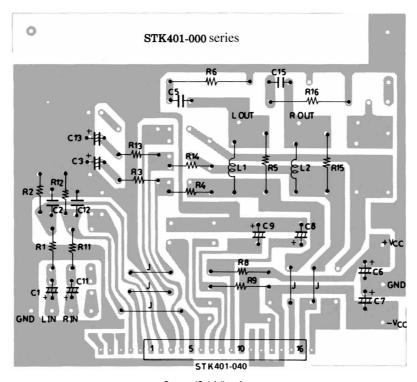Sample PCB Layout for 2-Channel or 3-Channel Amplifiers



Copper (Cu) foil surface
Pin 6 of STK400-000 series devices corresponds to pin 1 of STK401-000 series devices.

Sample Application Circuit

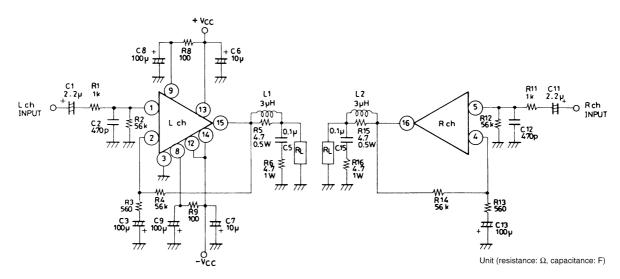

External Component Description


Input coupling capacitors. For DC blocking. Since capacitor reactance becomes larger at lower frequencies, the output noise can be adversely affected by signal source resistance-dependent 1ft noise. In this case, a lower reactance value should be chosen. In order to remove pop noise at power-on, larger values of capacitance should be chosen for C1 and C11, which determine the input time constant, and smaller values for C3 and C13 in the NF circuit. C2, C12 Input filter capacitors. These, together with R1 and R11, form filters to reduce high-frequency noise. NF capacitors. These determine the low-side cut-off frequency. f₁. = 1/2 π × C13(C13) × R3(R13) Large values should be chosen for C3 and C13 to maintain voltage gain at low frequencies. However, because this would tend to increase the shock noise at power-on, values larger than absolutely necessary should be avoided. C5, C15 Oscillation prevention capacitors. Mylar capacitors are recommended for their excellent thermal and frequency characteristics. Oscillation prevention capacitors. These should be inserted as close as possible to the IC supply pins to reduce supply impedance and hence provide stable IC operation. Electrolytic capacitors are recommended. Decoupling capacitors. These objective with R3 and R9, form time constant circuits that remove shock noise and ripple voltage from the supply, preventing any noise being coupled to the inputs. R1, R11 Input filter resistors. R2, R12 Input filter resistors. N2 = 408 is recommended using R3, R13 = 5602, and R4, R14 = 56kΩ Gain adjustments are best made using R3 and R13. If gain adjustments are made using R4 and R14, then set R2, R12 = R4, R14 to maintain V _N balance stability. R5, R15 Oscillation prevention resistors. P R6(R16) = (V _{CC} max/√2)/(1/2πf x C5(C15) + R6(R16)) × R6(R16) where f1 is the output signal frequency upper limit. Ripple filter resistors. P P mx, ripple regiscion and supply power-on shock noise are all affected by this resistance. These resistors should be chosen taking int		
These, together with R1 and R11, form filters to reduce high-frequency noise. NF capacitors. These determine the low-side cut-off frequency. f _L = \frac{1}{2π \times C1(C13) \times R3(R13)} Large values should be chosen for C3 and C13 to maintain voltage gain at low frequencies. However, because this would tend to increase the shock noise at power-on, values larger than absolutely necessary should be avoided. C5, C15 Oscillation prevention capacitors. Mylar capacitors are recommended for their excellent thermal and frequency characteristics. Oscillation prevention capacitors. These should be inserted as close as possible to the IC supply pins to reduce supply impedance and hence provide stable IC operation. Electrolytic capacitors are recommended. Decoupling capacitors. These should be inserted as close as possible to the IC supply pins to reduce supply impedance and hence provide stable IC operation. Electrolytic capacitors. These should be inserted as close as possible to the IC supply pins to reduce supply impedance and hence provide stable IC operation. Electrolytic capacitors. These should be inserted as close as possible to the IC supply pins to reduce supply impedance and hence provide stable IC operation. Electrolytic capacitors. These should be inserted as close as possible to the IC supply pins to reduce supply impedance and hence provide stable IC operation. R1, R11 Input filter resistors. R2, R12 Input bias resistors. These are used to bias the input pins at zero potential. The input impedance is largely determined by this resistance. Voltage-gain VG setting resistors. Voltage-gain VG setting resistors. Voltage-gain VG setting resistors. Voltage-gain VG setting resistors. Oscillation prevention resistors. The power dissipated in these resistors is dependent on the frequency, as given below. P R6(R16) = \frac{V_C max/\sqrt{2}{V_C max/\sqrt{2}}^2 \times R6(R16)} Where f is the output signal frequency upper limit. Ripple filter resistors. P ₀ max, ripple rejection and supply power-on shoc	C1, C11	For DC blocking. Since capacitor reactance becomes larger at lower frequencies, the output noise can be adversely affected by signal source resistance-dependent 1/f noise. In this case, a lower reactance value should be chosen. In order to remove pop noise at power-on, larger values of capacitance should be chosen for C1 and C11, which determine the input time constant, and smaller values for C3 and C13 in the
These determine the low-side cut-off frequency. f _L = 1/(2π × C 3 (C13) × R 3 (R 13)) Large values should be chosen for C3 and C13 to maintain voltage gain at low frequencies. However, because this would tend to increase the shock noise at power-on, values larger than absolutely necessary should be avoided. C5, C15 Oscillation prevention capacitors. Mylar capacitors are recommended for their excellent thermal and frequency characteristics. Oscillation prevention capacitors. These should be inserted as close as possible to the IC supply pins to reduce supply impedance and hence provide stable IC operation. Electrolytic capacitors are recommended. C8, C9 Decoupling capacitors. These should be inserted as close as possible to the IC supply pins to reduce supply impedance and hence provide stable IC operation. Electrolytic capacitors are recommended. Electrolytic capacitors. These should be inserted as close as possible to the IC supply pins to reduce supply impedance and hence provide stable IC operation. Electrolytic capacitors. These should be inserted as close as possible to the IC supply pins to reduce supply impedance and hence provide stable IC operation. Electrolytic capacitors. These, together with R8 and R9, form time constant circuits that remove shock noise and ripple voltage from the supply, preventing any noise being coupled to the inputs. R1, R11 Input filter resistors. Notage-gain VG setting resistors. Voltage-gain VG setting resistors. Voltage-gain VG setting resistors. Voltage-gain VG setting resistors. Voltage-gain VG setting resistors. Oscillation prevention resistors. The power dissipated in these resistors is dependent on the frequency, as given below. P R6(R16) = (V _{CC} max/√2 / (1/2πf × C6(C15) + R6(R16)) where f is the output signal frequency upper limit. R8, R9 R9, R9 R6, R16 R8, R9 R9, R9 R6, R16 Oscillation prevention coils.	C2, C12	
Mylar capacitors are recommended for their excellent thermal and frequency characteristics. Oscillation prevention capacitors. These should be inserted as close as possible to the IC supply pins to reduce supply impedance and hence provide stable IC operation. Electrolytic capacitors are recommended. Decoupling capacitors. These, together with R8 and R9, form time constant circuits that remove shock noise and ripple voltage from the supply, preventing any noise being coupled to the inputs. R1, R11 Input filter resistors. R2, R12 Input bias resistors. These are used to bias the input pins at zero potential. The input impedance is largely determined by this resistance. Voltage-gain VG setting resistors. VG = 40dB is recommended using R3, R13 = 560Ω, and R4, R14 = 56kΩ. Gain adjustments are best made using R3 and R13. If gain adjustments are made using R4 and R14, then set R2, R12 = R4, R14 to maintain V _N balance stability. R5, R15 Oscillation prevention resistors. Oscillation prevention resistors. The power dissipated in these resistors is dependent on the frequency, as given below. R6, R16 PR6(R16) = (V _{CC} max/√2)/(1/2πf × C5(C15) + R6(R16)) ² × R6(R16) where f is the output signal frequency upper limit. Ripple filter resistors. P _O max, ripple rejection and supply power-on shock noise are all affected by this resistance. These resistors should be chosen taking into consideration both the function they perform as predriver transistor limiting resistors during load short circuits and the peak current that flows through them when charging C8 and C9. Oscillation prevention coils.	C3, C13	These determine the low-side cut-off frequency. $f_L = \frac{1}{2\pi \times C3(C13) \times R3(R13)}$ Large values should be chosen for C3 and C13 to maintain voltage gain at low frequencies. However, because this would tend to increase the
These should be inserted as close as possible to the IC supply pins to reduce supply impedance and hence provide stable IC operation. Electrolytic capacitors are recommended. C8, C9 Decoupling capacitors. These, together with R8 and R9, form time constant circuits that remove shock noise and ripple voltage from the supply, preventing any noise being coupled to the inputs. R1, R11 Input filter resistors. R2, R12 Input bias resistors. These are used to bias the input pins at zero potential. The input impedance is largely determined by this resistance. Voltage-gain VG setting resistors. VG = 40dB is recommended using R3, R13 = 560Ω, and R4, R14 = 56kΩ. Gain adjustments are best made using R3 and R13. If gain adjustments are made using R4 and R14, then set R2, R12 = R4, R14 to maintain V _N balance stability. R5, R15 Oscillation prevention resistors. Oscillation prevention resistors. The power dissipated in these resistors is dependent on the frequency, as given below. R6, R16 P R6(R16) = (V _{CC} max/√2)/(1/2πf × C5(C15) + R6(R16)) ² × R6(R16) where f is the output signal frequency upper limit. Ripple filter resistors. P _O max, ripple rejection and supply power-on shock noise are all affected by this resistance. These resistors should be chosen taking into consideration both the function they perform as predriver transistor limiting resistors during load short circuits and the peak current that flows through them when charging C8 and C9.	C5, C15	
These, together with R8 and R9, form time constant circuits that remove shock noise and ripple voltage from the supply, preventing any noise being coupled to the inputs. R1, R11 Input filter resistors. R2, R12 Input bias resistors. These are used to bias the input pins at zero potential. The input impedance is largely determined by this resistance. Voltage-gain VG setting resistors. VG = 40dB is recommended using R3, R13 = 560Ω , and R4, R14 = $56k\Omega$. Gain adjustments are best made using R3 and R13. If gain adjustments are made using R4 and R14, then set R2, R12 = R4, R14 to maintain V_N balance stability. R5, R15 Oscillation prevention resistors. Oscillation prevention resistors. The power dissipated in these resistors is dependent on the frequency, as given below. R6, R16 $P R6(R16) = \left(\frac{V_{CC} \max \sqrt{2}}{1/2\pi f \times C5(C15) + R6(R16)}\right)^2 \times R6(R16)$ where f is the output signal frequency upper limit. Ripple filter resistors. Po max, ripple rejection and supply power-on shock noise are all affected by this resistance. These resistors should be chosen taking into consideration both the function they perform as predriver transistor limiting resistors during load short circuits and the peak current that flows through them when charging C8 and C9. Oscillation prevention coils.	C6, C7	These should be inserted as close as possible to the IC supply pins to reduce supply impedance and hence provide stable IC operation.
R2, R12 Input bias resistors. These are used to bias the input pins at zero potential. The input impedance is largely determined by this resistance. R3, R13 R4, R14 Voltage-gain VG setting resistors. VG = 40dB is recommended using R3, R13 = 560Ω , and R4, R14 = $56k\Omega$. Gain adjustments are best made using R3 and R13. If gain adjustments are made using R4 and R14, then set R2, R12 = R4, R14 to maintain V _N balance stability. R5, R15 Oscillation prevention resistors. Oscillation prevention resistors. The power dissipated in these resistors is dependent on the frequency, as given below. R6, R16 $P R6(R16) = \left(\frac{V_{CC} \max \sqrt{2}}{1/2\pi f \times C5(C15) + R6(R16)}\right)^2 \times R6(R16)$ where f is the output signal frequency upper limit. Ripple filter resistors. P _O max, ripple rejection and supply power-on shock noise are all affected by this resistance. These resistors should be chosen taking into consideration both the function they perform as predriver transistor limiting resistors during load short circuits and the peak current that flows through them when charging C8 and C9. Oscillation prevention coils.	C8, C9	These, together with R8 and R9, form time constant circuits that remove shock noise and ripple voltage from the supply, preventing any noise
These are used to bias the input pins at zero potential. The input impedance is largely determined by this resistance. R3, R13	R1, R11	Input filter resistors.
R3, R13 R4, R14 VG = 40dB is recommended using R3, R13 = 560Ω, and R4, R14 = 56kΩ. Gain adjustments are best made using R3 and R13. If gain adjustments are made using R4 and R14, then set R2, R12 = R4, R14 to maintain V _N balance stability. R5, R15 Oscillation prevention resistors. Oscillation prevention resistors. The power dissipated in these resistors is dependent on the frequency, as given below. PR6(R16) = $\left(\frac{V_{CC} \max \sqrt{2}}{1/2\pi f \times C5(C15) + R6(R16)}\right)^2 \times R6(R16)$ where f is the output signal frequency upper limit. Ripple filter resistors. P _O max, ripple rejection and supply power-on shock noise are all affected by this resistance. These resistors should be chosen taking into consideration both the function they perform as predriver transistor limiting resistors during load short circuits and the peak current that flows through them when charging C8 and C9.	R2, R12	
Oscillation prevention resistors. The power dissipated in these resistors is dependent on the frequency, as given below. $P = R6(R16) = \left(\frac{V_{CC} \text{ max}/\sqrt{2}}{1/2\pi f \times C5(C15) + R6(R16)}\right)^2 \times R6(R16)$ where f is the output signal frequency upper limit. Ripple filter resistors. $P_{O} = R8, R9$ R8, R9 R8, R9 R8, R9 R8, R9 Oscillation prevention and supply power-on shock noise are all affected by this resistance. These resistors should be chosen taking into consideration both the function they perform as predriver transistor limiting resistors during load short circuits and the peak current that flows through them when charging C8 and C9. Oscillation prevention coils.		VG = 40dB is recommended using R3, R13 = 560Ω , and R4, R14 = $56k\Omega$. Gain adjustments are best made using R3 and R13. If gain
The power dissipated in these resistors is dependent on the frequency, as given below. P R6(R16) = $\left(\frac{V_{CC} \text{ max}/\sqrt{2}}{1/2\pi f \times C5(C15) + R6(R16)}\right)^2 \times R6(R16)$ where f is the output signal frequency upper limit. Ripple filter resistors. Po max, ripple rejection and supply power-on shock noise are all affected by this resistance. These resistors should be chosen taking into consideration both the function they perform as predriver transistor limiting resistors during load short circuits and the peak current that flows through them when charging C8 and C9. Oscillation prevention coils.	R5, R15	Oscillation prevention resistors.
R8, R9 Po max, ripple rejection and supply power-on shock noise are all affected by this resistance. These resistors should be chosen taking into consideration both the function they perform as predriver transistor limiting resistors during load short circuits and the peak current that flows through them when charging C8 and C9. Oscillation prevention coils.	R6, R16	The power dissipated in these resistors is dependent on the frequency, as given below. $P \ R6(R16) = \left(\frac{V_{CC} \ max/\sqrt{2}}{1/2\pi f \times C5(C15) + R6(R16)}\right)^2 \times R6(R16)$
	R8, R9	Po max, ripple rejection and supply power-on shock noise are all affected by this resistance. These resistors should be chosen taking into consideration both the function they perform as predriver transistor limiting resistors during load short circuits and the peak current that flows
These correct the phase difference caused by capacitive loads and increase stability against oscillation.	L1, L2	Oscillation prevention coils. These correct the phase difference caused by capacitive loads and increase stability against oscillation.

Series Configuration


3-channel Rated amplifier type Nos.	Rated 2-channel	Rated	THD [%] f = 20Hz to 20kHz	Supply voltage [V] ¹				
	amplifier type Output	output		V _{CC} max1	V _{CC} max2	V _{CC} 1	V _{CC} 2	
STK400-010	10W×3	STK401-010	10W×2		-	±26	±17	±14
STK400-020	15W×3	STK401-020	15W×2		-	±29	±20	±16
STK400-030	20W×3	STK401-030	20W×2		-	±34	±23	±19
STK400-040	25W×3	STK401-040	25W×2		-	±36	±25	±21
STK400-050	30W×3	STK401-050	30W×2		-	±39	±26	±22
STK400-060	35W×3	STK401-060	35W×2		-	±41	±28	±23
STK400-070	40W×3	STK401-070	40W×2	0.4	-	±44	±30	<u>+2</u> 4
STK400-080	45W×3	STK401-080	45W×2	0.4	-	±45	±31	±25
STK400-090	50W×3	STK401-090	50W×2		-	±47	±32	±26
STK400-100	60W×3	STK401-100	60W×2		-	±51	±35	<u>+2</u> 7
STK400-110	70W×3	STK401-110	70W×2		±56.0	-	±38	-
-	-	STK401-120	80W×2		±61.0	-	±42	-
-	-	STK401-130	100W×2		±65.0	-	±45	-
-	-	STK401-140	120W × 2		±74.0	-	±51	_

^{1.} V_{CC} max1 (R_L = 6Ω), V_{CC} max2 (R_L = 3 to 6Ω), V_{CC} 1 (R_L = 6Ω), V_{CC} 2 (R_L = 3Ω)

Sample Designs using a Common PCB

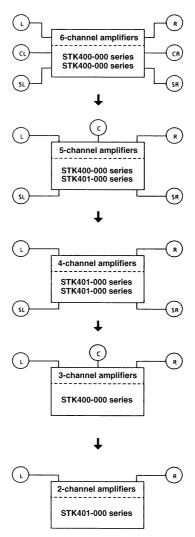

External Circuit Diagram

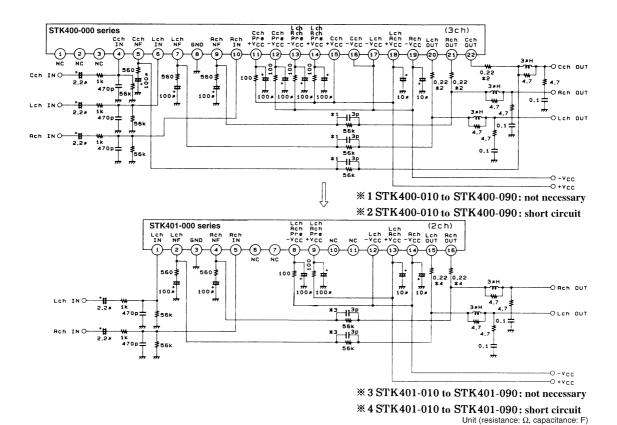

Heatsink Design Considerations

The heatsink thermal resistance, θ c-a, required to dissipate the STK401-040 device total power dissipation, Pd, is determined as follows:

Condition 1: IC substrate temperature not to exceed 125°C.

$$Pd \times \theta c-a + Ta < 125^{\circ}C$$
(1)

where Ta is the guaranteed maximum ambient temperature

Condition 2: Power transistor junction temperature, Tj, not to exceed 150°C.

$$Pd \times \theta c - a + Pd/N \times \theta j - c + Ta < 150^{\circ}C$$
(2)

where N is the number of power transistors and θ j-c is the power transistor thermal resistance per transistor. Note that the power dissipated per transistor is the total, Pd, divided evenly among the N power transistors.

Expressions (1) and (2) can be rewritten making θ c-a the subject.

$$\theta c$$
-a < (125 – Ta)/Pd.....(1)'

$$\theta c-a < (150 - Ta)/Pd - \theta j-c/N \dots (2)'$$

The heatsink required must have a thermal resistance that simultaneously satisfies both expressions.

The heatsink thermal resistance can be determined from (1)' and (2)' once the following parameters have been defined.

- · Supply voltage
- · Load resistance
- Guaranteed maximum ambient temperature

The total device power dissipation when STK401-040 $V_{CC} = \pm 25V$ and $R_L = 6\Omega$, for a continuous sine wave signal, is a maximum of 44W, as shown in Figure 1.

When estimating the power dissipation for an actual audio signal input, the rule of thumb is to select Pd corresponding to $1/10~P_{\rm O}$ max (within safe limits) for a continuous sine wave input. For example, from Figure 1,

$$Pd = 25.5W$$
 (for $1/10 P_O max = 2.5W$)

The STK401-040 has 4 power transistors, and the thermal resistance per transistor, θ j-c, is 2.1°C/W. If the guaranteed maximum ambient temperature, Ta, is 50°C, then the required heatsink thermal resistance, θ c-a, is:

From expression (1)':
$$\theta$$
c-a < (125 – 50)/25.5 < 2.94

From expression (2)':
$$\theta$$
c-a < (150 – 50)/25.5 – 2.1/4
< 3.39


Therefore, to satisfy both expressions, the required heatsink must have a thermal resistance less than 2.94°C/W. Similarly, when STK401-040 V_{CC} = $\pm 21V$ and R_L = $3\Omega,$ from Figure 2:


 $Pd = 30.6W \text{ (for } 1/10 P_{O} \text{ max} = 2.5W)$


From expression (1)': θ c-a < (125 – 50)/30.6 < 2.45


From expression (2)': θ c-a < (150 - 50)/30.6 - 2.1/4< 2.74 Therefore, to satisfy both expressions, the required heat-sink must have a thermal resistance less than 2.45°C/W.

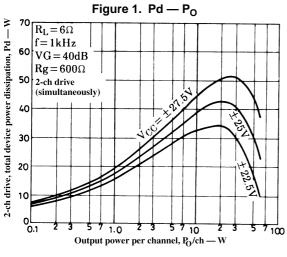
This heatsink design example is based on a constant-voltage supply, and should be verified within your specific set environment.




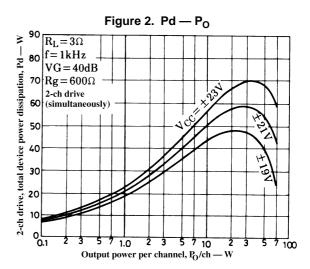


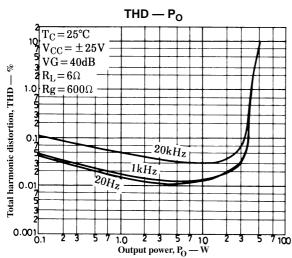

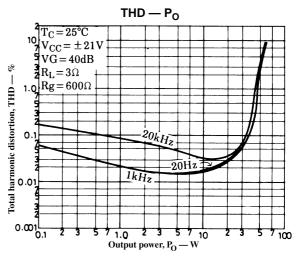

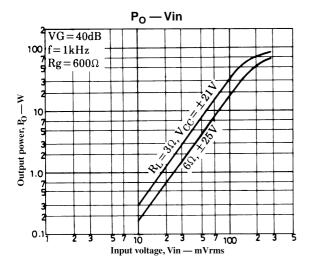

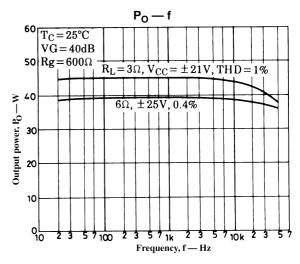

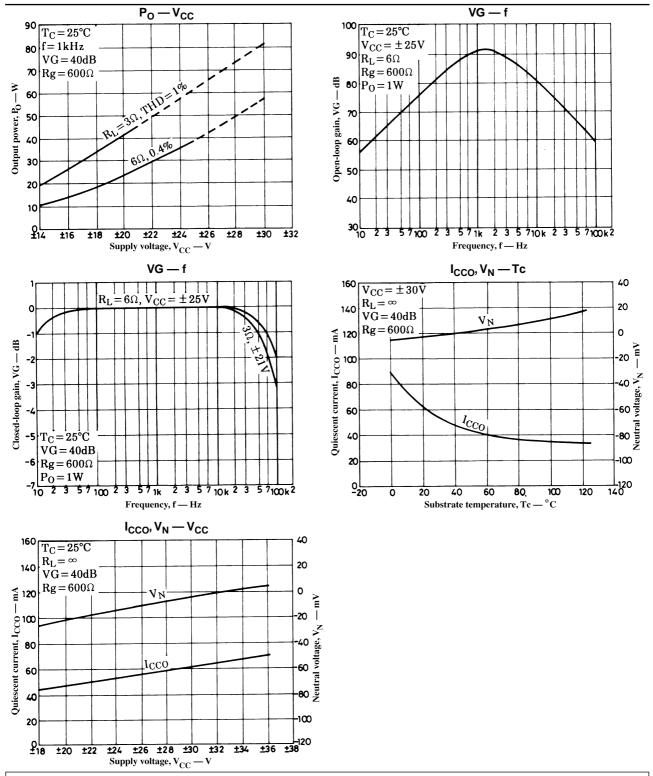

- No products described or contained herein are intended for use in surgical implants, life-support systems, aerospace equipment, nuclear power control systems, vehicles, disaster/crime-prevention equipment and the like, the failure of which may directly or indirectly cause injury, death or property loss.
- Anyone purchasing any products described or contained herein for an above-mentioned use shall:
 - Accept full responsibility and indemnify and defend SANYO ELECTRIC CO., LTD., its affiliates, subsidiaries and distributors and all their officers and employees, jointly and severally, against any and all claims and litigation and all damages, cost and expenses associated with such use:
 - Not impose any responsibility for any fault or negligence which may be cited in any such claim or litigation on SANYO ELECTRIC CO., LTD., its affiliates, subsidiaries and distributors or any of their officers and employees, jointly or severally.
- Information (including circuit diagrams and circuit parameters) herein is for example only; it is not guaranteed for volume production. SANYO believes information herein is accurate and reliable, but no guarantees are made or implied regarding its use or any infringements of intellectual property rights or other rights of third parties.